

# IMPLEMENTATION OF SEQUENCE DETECTORS BY FINITE STATE MACHINES USING VERILOG

A series of five parallel diagonal lines in a light blue color, extending from the bottom left towards the top right, positioned to the right of the main title.

## Table of Contents

<b>FSM DESIGN STYLES.....</b>	<b>1</b>
SINGLE PROCEDURAL BLOCK.....	1
TWO PROCEDURAL BLOCK(METHOD-01).....	6
TWO PROCEDURAL BLOCK(METHOD-02).....	11
THREE PROCEDURAL BLOCK.....	16
<b>1010 SEQUENCE DETECTOR NON OVERLAPPING USING MEALY MACHINE .....</b>	<b>21</b>
<b>1010 SEQUENCE DETECTOR OVERLAPPING USING MEALY MACHINE .....</b>	<b>26</b>
<b>1010 SEQUENCE DETECTOR NON OVERLAPPING USING MOORE MACHINE .....</b>	<b>31</b>
<b>1010 SEQUENCE DETECTOR OVERLAPPING USING MOORE MACHINE .....</b>	<b>36</b>
<b>101X SEQUENCE DETECTOR OVERLAPPING USING MEALY MACHINE .....</b>	<b>41</b>
<b>10X0 SEQUENCE DETECTOR OVERLAPPING USING MEALY MACHINE .....</b>	<b>46</b>

## SINGLE PROCEDURAL BLOCK

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over(Clk,Rst,In,OP,state);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]state;

reg op;    // register to store output
reg [1:0]State; // State register

parameter s0    = 0; // State registers
parameter s1    = 1;
parameter s10   = 2;
parameter s101  = 3;

always @(posedge Clk,negedge Rst) begin
    if(!Rst)
    begin
        State <= s0;
        op <= 0;
    end

    else begin
        case(State)
            s0 : begin
                State <= In ? s1:s0 ;
                op <= 0;
            end

            s1 : begin
```

```
        State <= In ? s1:s10 ;
        op <= 0;
    end

    s10 : begin
        State <= In ? s101:s0 ;
        op <= 0;
    end

    s101: begin
        State <= In ? s1:s0 ;
        op <= In ? 0:1 ;
    end

    default : begin
        State <= s0 ;
        op <= 0;
    end
endcase
end

end

assign OP = op;
assign state = State;

endmodule
```

## **TESTBENCH MODULE**

```
`timescale 1ns / 1ps
module mealy_1010_seq_det_non_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [1:0]state;
//instantiating design to test
mealy_1010_seq_det_non_over UUT(Clk,Rst,In,OP,state);

// Monitoring the simulation results
initial begin
    $monitor("Input = %b || State = %b || Output = %b",In,state,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In = 1'b1;
    #10 In = 1'b0;
    #10 In = 1'b0;
    #10 In = 1'b1;
    #10 In = 1'b0;
    #10 In = 1'b0;
```

```


#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS

 

## SIMULATION OUTPUTS

```
Input = 1 || State = 00 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 0
Input = 0 || State = 00 || Output = 1
Input = 1 || State = 00 || Output = 1
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 0
Input = 0 || State = 00 || Output = 1
Input = 0 || State = 00 || Output = 0
```

## TWO PROCEDURAL BLOCK(METHOD-01)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over(Clk,Rst,In,OP);
input Clk,Rst,In; // Input signals
output OP;        // Output signal

reg op;    // register to store output
reg [1:0]C_State,N_State; // state register

parameter  s0    = 0, // state registers
            s1    = 1,
            s10   = 2,
            s101  = 3;

always @(posedge Clk,negedge Rst) begin
    if(!Rst)
    begin
        C_State <= s0;
        op <= 0;
    end

    else begin
        C_State <= N_State;
    end
end

always @(C_State,In) begin

    case(C_State)
```



```
s0 :    begin N_State <= In ? s1:s0 ; op <= 0 ; end

s1 :    begin N_State <= In ? s1:s10 ; op <= 0 ; end

s10 :   begin N_State <= In ? s101:s0 ; op <= 0 ; end

s101 :  begin  N_State <= In ? s1:s0 ; op <= In ? 0:1 ;
end

      default : begin N_State <= s0; op <= 0; end

    endcase

  end

assign OP = op;

endmodule
```

## **TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;

//instantiating design to test
mealy_1010_seq_det_non_over UUT(Clk,Rst,In,OP);

// Monitoring the simulation results
initial begin
```


```
$monitor("CS = %d || Input = %b || NS = %b || Output  
= %b",UUT.C_State,In,UUT.N_State,OP);  
end  
  
// clock signal generation  
initial begin  
    Clk = 1'b0;  
    forever #5 Clk = ~Clk;  
end  
  
// input signals  
initial begin  
    Rst = 1'b0;  
    #15 Rst = 1'b1;  
end  
  
initial begin  
    #10 In  = 1'b0;  
    #10 In  = 1'b0;  
    #10 In  = 1'b1;  
    #10 In  = 1'b0;  
    #10 In  = 1'b0;  
    #10 In  = 1'b1;  
    #10 In  = 1'b0;  
    #10 In  = 1'b1;  
    #7   In  = 1'b0;  
    #13 In  = 1'b1;  
    #8   In  = 1'b0;  
    #10 In  = 1'b1;  
    #10 In  = 1'b1;  
    #10 In  = 1'b0;  
    #10 In  = 1'b1;  
    #10 In  = 1'b0;
```

```
#10 In  = 1'b0;  
#10 $finish();
```

```
end
```

```
endmodule
```

SIMULATION WAVEFORMS

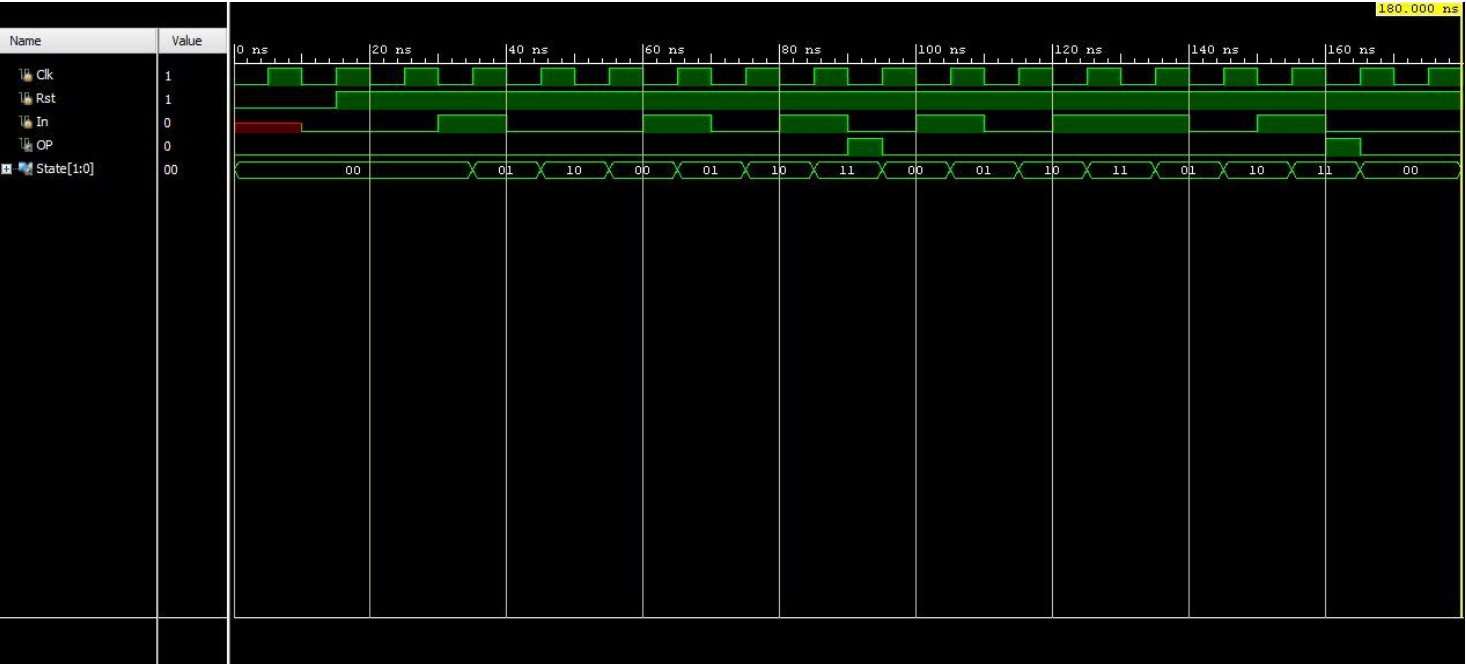

**SIMULATION OUTPUTS**

```
Input = x || State = 00 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 1
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 1
Input = 0 || State = 00 || Output = 0
```

## TWO PROCEDURAL BLOCK(METHOD-02)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over(Clk,Rst,In,OP,sta);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]sta;

reg op;    // register to store output
reg [1:0]state; // state register

parameter  s0    = 0, // state registers
            s1    = 1,
            s10   = 2,
            s101  = 3;

reg [1:0]State;

always @(posedge Clk,negedge Rst) begin
    if(!Rst)
    begin
        State <= s0;
        op <= 0;
    end

    else begin

        case(State)

            s0 :    State <= In ? s1:s0 ;

            s1 :    State <= In ? s1:s10 ;
```

```
        s10 :      State <= In ? s101:s0 ;

        s101 :      State <= In ? s1:s0 ;

        default :  State <= s0;

    endcase

end

end

always @(State,In) begin

    case(State)
        s0 :      op <= 0;

        s1 :      op <= 0;

        s10 :     op <= 0;

        s101:     op <= In ? 0:1 ;

        default : op <= 0;

    endcase

end

assign OP = op;
assign sta = State;

endmodule
```

**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [1:0]State;
//instantiating design to test
mealy_1010_seq_det_non_over UUT(Clk,Rst,In,OP,State);

// Monitoring the simulation results
initial begin
    $monitor("Input = %b || State = %b || Output = %b",In,State,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
```

```


#10 In      = 1'b1;
#10 In      = 1'b0;
#10 In      = 1'b1;
#10 In      = 1'b0;
#10 In      = 1'b1;
#10 In      = 1'b1;
#10 In      = 1'b0;
#10 In      = 1'b1;
#10 In      = 1'b0;
#10 In      = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS

 



**SIMULATION OUTPUTS**

```
Input = x || State = 00 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 1
Input = 0 || State = 00 || Output = 0
Input = 1 || State = 00 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 1 || State = 01 || Output = 0
Input = 0 || State = 01 || Output = 0
Input = 0 || State = 10 || Output = 0
Input = 1 || State = 10 || Output = 0
Input = 1 || State = 11 || Output = 0
Input = 0 || State = 11 || Output = 1
Input = 0 || State = 00 || Output = 0
```

## THREE PROCEDURAL BLOCK

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over(Clk,Rst,In,OP,cs,ns);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]cs,ns;

reg op;    // register to store output
reg state; // state register

parameter  s0    = 0, // state registers
            s1    = 1,
            s10   = 2,
            s101  = 3;

reg [1:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
        op <= 0;
    end

    else begin
        C_State <= N_State;
    end
end

// Next state logic
```

```
always @(C_State,In) begin

    case(C_State)

        s0 : N_State <= In ? s1:s0 ;

        s1 : N_State <= In ? s1:s10 ;

        s10 : N_State <= In ? s101:s0 ;

        s101: N_State <= In ? s1:s0 ;

        default : N_State <= s0;

    endcase
end

// Output logic

always @(C_State,In) begin
    case(C_State)

        s0 : op <= 0;

        s1 : op <= 0;

        s10 : op <= 0;

        s101: op <= In ? 0:1 ;

        default : op <= 0;

    endcase
end
```

```
//  
assign OP = op;  
assign cs = C_State;  
assign ns = N_State;  
  
endmodule
```

## **TESTBENCH MODULE**

```
`timescale 1ns / 1ps  
module mealy_1010_seq_det_non_over_tb ();  
    // Signal Declarations  
    reg Clk,Rst,In;  
    wire OP;  
    wire [1:0]CS,NS;  
    //instantiating design to test  
    mealy_1010_seq_det_non_over UUT(Clk,Rst,In,OP,CS,NS);  
  
    // Monitoring the simulation results  
    initial begin  
        $monitor("Current State = %b || Input = %b || Next State = %b ||  
Output = %b",UUT.C_State,In,UUT.N_State,OP);  
    end  
  
    // clock signal generation  
    initial begin  
        Clk = 1'b0;  
        forever #5 Clk = ~Clk;  
    end  
  
    // input signals  
    initial begin  
        Rst = 1'b0;
```

```
#15 Rst = 1'b1; end

initial begin

    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #7   In  = 1'b0;
    #13 In  = 1'b1;
    #8   In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 $finish();

end

endmodule
```

## SIMULATION WAVEFORMS



## SIMULATION OUTPUTS

```

Current State = 00 || Input = x || Next State = 0x || Output = 0
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 11 || Input = 0 || Next State = 00 || Output = 1
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 11 || Input = 0 || Next State = 00 || Output = 1
Current State = 00 || Input = 0 || Next State = 00 || Output = 0

```

# SEQUENCE DETECTOR 1010 USING MEALY MACHINE

## (NON OVERLAPPING)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over(Clk,Rst,In,OP,cs,ns);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]cs,ns; // To represent the present and next states

parameter s0 = 0, // state registers
           s1 = 1,
           s10 = 2,
           s101 = 3;

reg [1:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end

// Next state logic
```

```
always @(C_State,In) begin

    case (C_State)

        s0   : N_State <= In ? s1:s0 ;

        s1   : N_State <= In ? s1:s10 ;

        s10  : N_State <= In ? s101:s0 ;

        s101: N_State <= In ? s1:s0 ;

        default : N_State <= s0;

    endcase
end

// Output logic

assign OP = ((C_State == s101 ) && (!In) );


assign cs = C_State;
assign ns = N_State;

endmodule
```



**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_non_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [1:0]CS,NS;
//instantiating design to test
mealy_1010_seq_det_non_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("Current State = %b || Input = %b || Next State = %b ||
Output = %b",UUT.C_State,In,UUT.N_State,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end
initial begin
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
```

```


#10 In  = 1'b1;
#7  In  = 1'b0;
#13 In  = 1'b1;
#8   In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS

 

**SIMULATION OUTPUTS**

```

Current State = 00 || Input = x || Next State = 0x || Output = 0
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 11 || Input = 0 || Next State = 00 || Output = 1
Current State = 00 || Input = 0 || Next State = 00 || Output = 0
Current State = 00 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 1 || Next State = 01 || Output = 0
Current State = 01 || Input = 0 || Next State = 10 || Output = 0
Current State = 10 || Input = 0 || Next State = 00 || Output = 0
Current State = 10 || Input = 1 || Next State = 11 || Output = 0
Current State = 11 || Input = 1 || Next State = 01 || Output = 0
Current State = 11 || Input = 0 || Next State = 00 || Output = 1
Current State = 00 || Input = 0 || Next State = 00 || Output = 0

```

# SEQUENCE DETECTOR 1010 USING MEALY MACHINE

## (OVERLAPPING)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_over (Clk,Rst,In,OP,CS,NS);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]CS,NS;

parameter  s0    = 0, // state registers
            s1    = 1,
            s10   = 2,
            s101  = 3;

reg [1:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end
```

```
FSM
// Next state logic
```

SEQUENCE DETECTORS

```
always @(C_State,In) begin

    case(C_State)

        s0   : N_State <= In ? s1:s0 ;

        s1   : N_State <= In ? s1:s10 ;

        s10  : N_State <= In ? s101:s0 ;

        s101 : N_State <= In ? s1:s10 ;

        default : N_State <= s0;

    endcase
end

// Output logic

assign OP = ((C_State == s101) && (!In));

//states
assign CS = C_State ;
assign NS = N_State ;

endmodule
```

**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module mealy_1010_seq_det_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire CS,NS;

//instantiating design to test
mealy_1010_seq_det_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("Time = %0t ||Current State = %b || Input = %b || Next State
= %b || Output = %b", $time,CS,In,NS,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
```

```

#10 In  = 1'b0;
#10 In  = 1'b1;
#7  In  = 1'b0;
#13 In  = 1'b1;
#8  In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS



**SIMULATION OUTPUTS**

```
Time = 0 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 20000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 25000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 30000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Time = 35000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 50000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 55000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 60000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Time = 65000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 70000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 75000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 77000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Time = 85000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 90000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 95000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 98000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Time = 105000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 108000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 115000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 128000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Time = 135000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Time = 138000 ||Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Time = 145000 ||Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Time = 148000 ||Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Time = 155000 ||Current State = 0 || Input = 0 || Next State = 0 || Output = 0
```



# SEQUENCE DETECTOR 1010 USING MOORE MACHINE

## (NON OVERLAPPING)

### DESIGN MOUDLE

```
`timescale 1ns / 1ps

module moore_1010_seq_det_non_over(Clk,Rst,In,OP,CS,NS);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [2:0]CS,NS; // states

parameter s0    = 0 , // state registers
           s1    = 1 ,
           s10   = 2 ,
           s101  = 3 ,
           s1010 = 4 ;

reg [2:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end
```

```
FSM
// Next state logic
```

SEQUENCE DETECTORS

```
always @(C_State,In) begin

    case(C_State)

        s0      : N_State <= In ? s1:s0 ;

        s1      : N_State <= In ? s1:s10 ;

        s10     : N_State <= In ? s101:s0 ;

        s101    : N_State <= In ? s1:s1010 ;

        s1010   : N_State <= In ? s1 : s0 ;

        default : N_State <= s0;

    endcase
end

// Output logic

assign OP = (C_State == s1010) ;

//
assign CS = C_State ;
assign NS = N_State ;

endmodule
```

**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module moore_1010_seq_det_non_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [2:0] CS,NS;

//instantiating design to test
moore_1010_seq_det_non_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("Time = %0t || Current State = %b || Input = %b || Next
State = %b || Output = %b",$time,CS,In,NS,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
```

```


#10 In  = 1'b0;
#10 In  = 1'b1;
#7  In  = 1'b0;
#13 In  = 1'b1;
#8   In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS

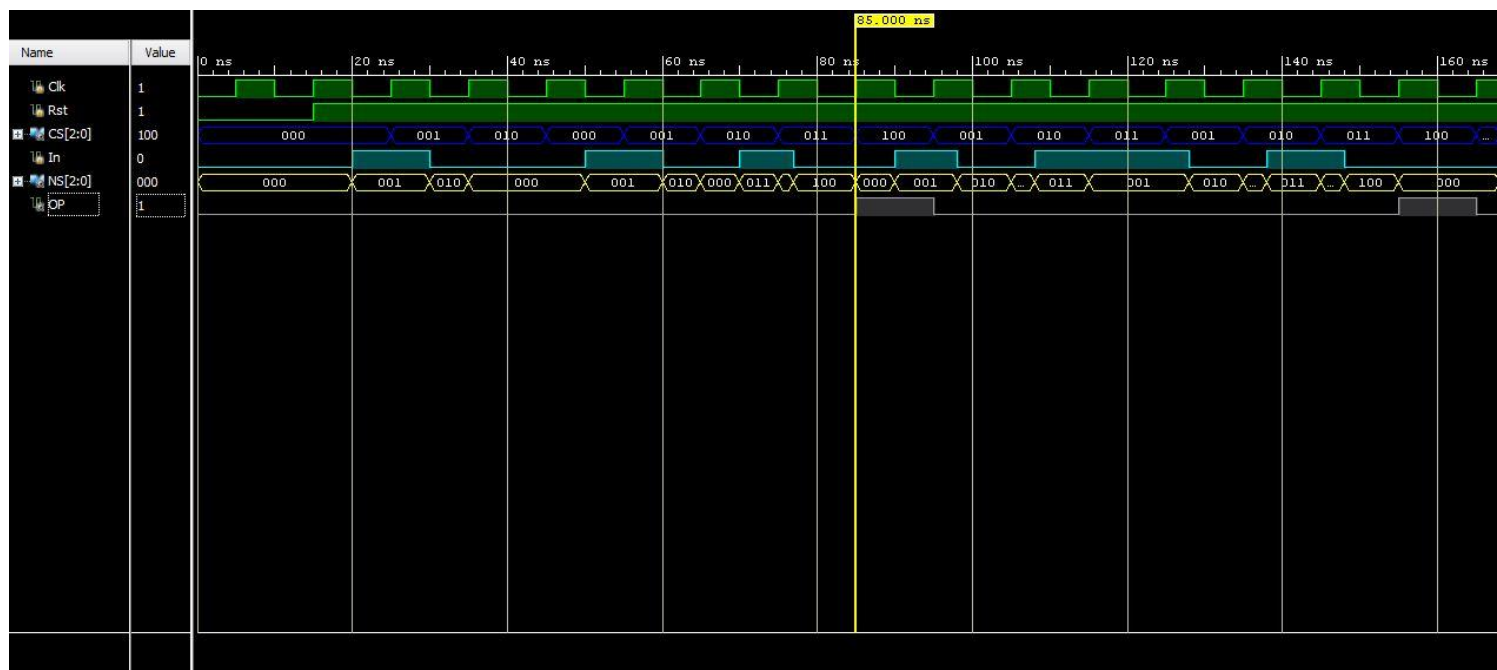

**SIMULATION OUTPUTS**

```
Time = 0 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
Time = 20000 || Current State = 000 || Input = 1 || Next State = 001 || Output = 0
Time = 25000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 30000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 35000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 45000 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
Time = 50000 || Current State = 000 || Input = 1 || Next State = 001 || Output = 0
Time = 55000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 60000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 65000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 70000 || Current State = 010 || Input = 1 || Next State = 011 || Output = 0
Time = 75000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 77000 || Current State = 011 || Input = 0 || Next State = 100 || Output = 0
Time = 85000 || Current State = 100 || Input = 0 || Next State = 000 || Output = 1
Time = 90000 || Current State = 100 || Input = 1 || Next State = 001 || Output = 1
Time = 95000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 98000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 105000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 108000 || Current State = 010 || Input = 1 || Next State = 011 || Output = 0
Time = 115000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 125000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 128000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 135000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 138000 || Current State = 010 || Input = 1 || Next State = 011 || Output = 0
Time = 145000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 148000 || Current State = 011 || Input = 0 || Next State = 100 || Output = 0
Time = 155000 || Current State = 100 || Input = 0 || Next State = 000 || Output = 1
Time = 165000 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
```

# SEQUENCE DETECTOR 1010 USING MOORE MACHINE

## (OVERLAPPING)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module moore_1010_seq_det_over(Clk,Rst,In,OP,CS,NS);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [2:0]CS,NS ;

parameter  s0    = 0 , // state registers
            s1    = 1 ,
            s10   = 2 ,
            s101  = 3 ,
            s1010 = 4 ;

reg [2:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end
```

```
FSM
// Next state logic
```

SEQUENCE DETECTORS

```
always @(C_State,In) begin
```

```
    case(C_State)
```

```
        s0      : N_State <= In ? s1 : s0 ;
```

```
        s1      : N_State <= In ? s1 : s10 ;
```

```
        s10     : N_State <= In ? s101 : s0 ;
```

```
        s101    : N_State <= In ? s1 : s1010 ;
```

```
        s1010   : N_State <= In ? s101 : s0 ;
```

```
        default : N_State <= s0;
```

```
    endcase
```

```
end
```

```
// Output logic
```

```
assign OP = (C_State == s1010);
```

```
//
```

```
assign CS = C_State ;
```

```
assign NS = N_State ;
```

```
endmodule
```

**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module moore_1010_seq_det_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [2:0]CS,NS;

//instantiating design to test
moore_1010_seq_det_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("Time = %0t || Current State = %b || Input = %b || Next
State = %b || Output = %b",$time,CS,In,NS,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
```



```

#10 In  = 1'b0;
#10 In  = 1'b1;
#7  In  = 1'b0;
#13 In  = 1'b1;
#8   In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS



**SIMULATION OUTPUTS**

```
Time = 0 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
Time = 20000 || Current State = 000 || Input = 1 || Next State = 001 || Output = 0
Time = 25000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 30000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 35000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 45000 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
Time = 50000 || Current State = 000 || Input = 1 || Next State = 001 || Output = 0
Time = 55000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 60000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 65000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 70000 || Current State = 010 || Input = 1 || Next State = 011 || Output = 0
Time = 75000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 77000 || Current State = 011 || Input = 0 || Next State = 100 || Output = 0
Time = 85000 || Current State = 100 || Input = 0 || Next State = 000 || Output = 1
Time = 90000 || Current State = 100 || Input = 1 || Next State = 011 || Output = 1
Time = 95000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 98000 || Current State = 011 || Input = 0 || Next State = 100 || Output = 0
Time = 105000 || Current State = 100 || Input = 0 || Next State = 000 || Output = 1
Time = 108000 || Current State = 100 || Input = 1 || Next State = 011 || Output = 1
Time = 115000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 125000 || Current State = 001 || Input = 1 || Next State = 001 || Output = 0
Time = 128000 || Current State = 001 || Input = 0 || Next State = 010 || Output = 0
Time = 135000 || Current State = 010 || Input = 0 || Next State = 000 || Output = 0
Time = 138000 || Current State = 010 || Input = 1 || Next State = 011 || Output = 0
Time = 145000 || Current State = 011 || Input = 1 || Next State = 001 || Output = 0
Time = 148000 || Current State = 011 || Input = 0 || Next State = 100 || Output = 0
Time = 155000 || Current State = 100 || Input = 0 || Next State = 000 || Output = 1
Time = 165000 || Current State = 000 || Input = 0 || Next State = 000 || Output = 0
```

## SEQUENCE DETECTOR 101X USING MEALY MACHINE

### (OVERLAPPING)

#### DESIGN MODULE

```
`timescale 1ns / 1ps

module mealy_101X_seq_det_over(Clk,Rst,In,OP,CS,NS);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [1:0]CS,NS; // states

parameter s0 = 0, // state registers
           s1 = 1,
           s10 = 2,
           s101 = 3;

reg [1:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end
```

```
FSM
// Next state logic
```

SEQUENCE DETECTORS

```
always @(C_State,In) begin
```

```
    case(C_State)
```

```
        s0   : N_State <= In ? s1:s0 ;
```

```
        s1   : N_State <= In ? s1:s10 ;
```

```
        s10  : N_State <= In ? s101:s0 ;
```

```
        s101: N_State <= In ? s1:s10 ;
```

```
        default : N_State <= s0;
```

```
    endcase
```

```
end
```

```
// Output logic
```

```
assign OP = ((C_State == s101) ? (In ? 1:1) : (In ? 0 : 0)) ;
```

```
//assing OP = (C_State == s101)  --> we can use it also for this sequence
Detector
```

```
//
```

```
assign CS = C_State ;
```

```
assign NS = N_State ;
```

```
endmodule
```

**TESTBENCH MODULE**

```
`timescale 1ns / 1ps

module mealy_101X_seq_det_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire CS,NS;

//instantiating design to test
mealy_101X_seq_det_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("Current State = %b || Input = %b || Next State = %b ||
Output = %b",CS,In,NS,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
```

```


#10 In  = 1'b0;
#10 In  = 1'b1;
#7  In  = 1'b0;
#13 In  = 1'b1;
# 8 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b1;
#10 In  = 1'b0;
#10 In  = 1'b0;
#10 $finish();

```

```
end
```

```
endmodule
```

## SIMULATION WAVEFORMS

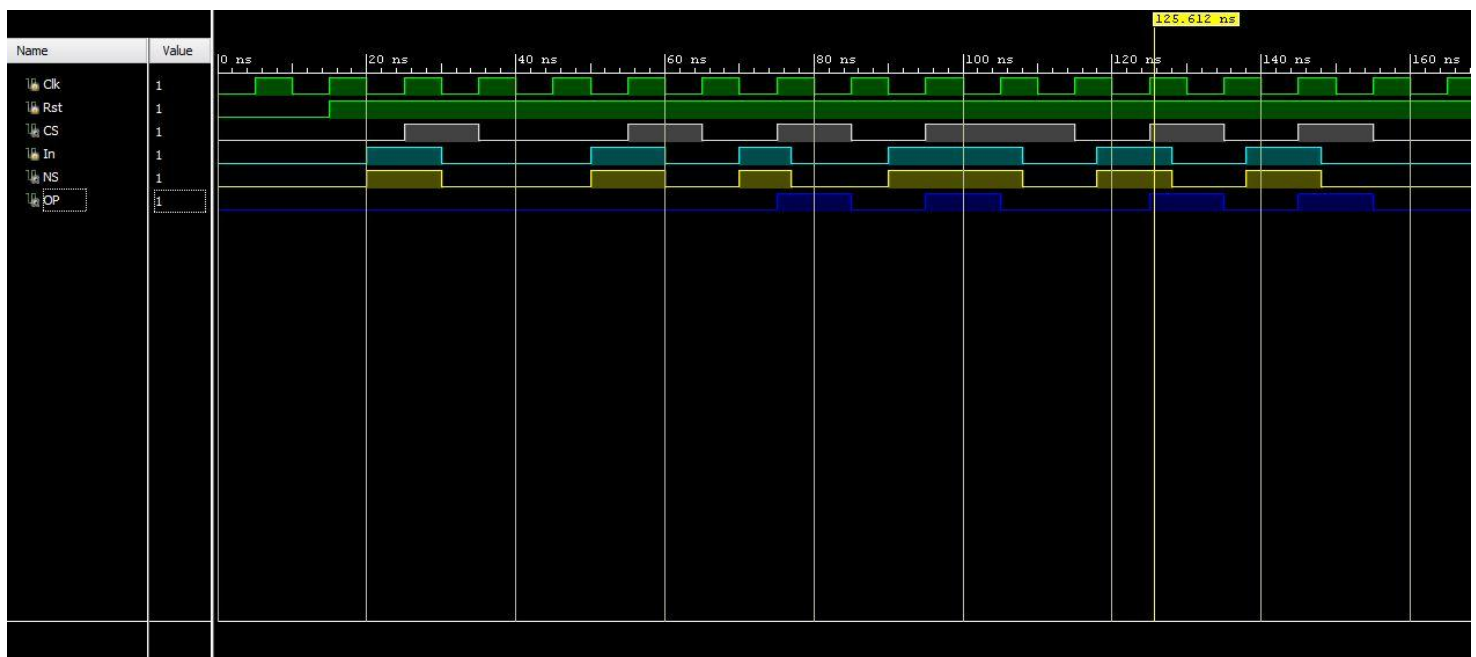

**SIMULATION OUTPUTS**

```
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 1
Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 1
Current State = 1 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 1
Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
Current State = 0 || Input = 1 || Next State = 1 || Output = 0
Current State = 1 || Input = 1 || Next State = 1 || Output = 1
Current State = 1 || Input = 0 || Next State = 0 || Output = 1
Current State = 0 || Input = 0 || Next State = 0 || Output = 0
```

# SEQUENCE DETECTOR 10X0 USING MOORE MACHINE

## (OVERLAPPING)

### DESIGN MODULE

```
`timescale 1ns / 1ps

module moore_10X0_seq_det_over(Clk,Rst,In,OP,CS,NS);
input Clk,Rst,In; // Input signals
output OP;        // Output signal
output [2:0]CS,NS; // states

parameter  s0      = 0 , // state registers
            s1      = 1 ,
            s10     = 2 ,
            s100    = 3 ,
            s101    = 4 ,
            s10X0   = 5 ;

reg x; // to know the 10X0--> X direction(1010/1000)

reg [2:0]C_State,N_State; // state declarations

// State register

always @(posedge Clk,negedge Rst) begin

    if(!Rst)
    begin
        C_State <= s0;
    end

    else begin
        C_State <= N_State;
    end
end
```



FSM  
// Next state logic

SEQUENCE DETECTORS

**always** @(C\_State,In) **begin**

**case** (C\_State)

        s0      : N\_State <= In ? s1 : s0 ;

        s1      : N\_State <= In ? s1 : s10 ;

        s10     : N\_State <= In ? s101 : s100 ;

        s100    : **begin** N\_State <= In ? s1 : s10X0 ;  x <= 0 ;**end**

        s101    : **begin** N\_State <= In ? s1 : s10X0 ;  x <= 1 ; **end**

        s10X0   : N\_State <= x ? (In ? s101 : s100 ) : (In ? s1 : s0 ) ;

**default** : N\_State <= s0;

**endcase**

**end**

// Output logic

**assign** OP = (C\_State == s10X0);

//

**assign** CS = C\_State ;

**assign** NS = N\_State ;

**endmodule**

**TESTBENCH MODULE**

```

`timescale 1ns / 1ps

module moore_10X0_seq_det_over_tb ();
// Signal Declarations
reg Clk,Rst,In;
wire OP;
wire [2:0]CS,NS;

//instantiating design to test
moore_10X0_seq_det_over UUT(Clk,Rst,In,OP,CS,NS);

// Monitoring the simulation results
initial begin
    $monitor("time = %0t || Current State = %b || Input = %b || Next
State = %b || Output = %b",$time,CS,In,NS,OP);
end

// clock signal generation
initial begin
    Clk = 1'b0;
    forever #5 Clk = ~Clk;
end

// input signals
initial begin
    Rst = 1'b0;
    #15 Rst = 1'b1; end

initial begin
    In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #7  In  = 1'b0;
    #13 In  = 1'b1;
    #8  In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b1;
    #10 In  = 1'b0;
    #10 In  = 1'b0;
    #10 $finish();
end
endmodule

```

